

CONTENT

Preface

vii

List of Abbreviations

xxiii

CHAPTER 1: Introduction to Microprocessors

1.1–1.54

- 1.1 Terms Used in Microprocessor Literature 1.1
- 1.2 Evolution of Microprocessors 1.3
- 1.3 Functional Building Blocks of a Microprocessor 1.6
- 1.4 Microprocessor-Based System (Organization of a Microcomputer) 1.7
 - 1.4.1 Concept of Multiplexing in a Microprocessor 1.8
 - 1.4.2 Demultiplexing of Address/Data Lines in an 8085 Microprocessor 1.9
 - 1.4.3 Demultiplexing of Address/Data Lines in an 8086 Microprocessor 1.9
- 1.5 INTEL 8085 Microprocessor 1.10
 - 1.5.1 Pin Configuration of an 8085 Microprocessor 1.11
 - 1.5.2 Driving X_1 and X_2 Inputs in an 8085 Microprocessor 1.14
 - 1.5.3 Hardware Architecture of an 8085 Microprocessor 1.15
 - 1.5.4 Instruction Execution and Data Flow in an 8085 Microprocessor 1.17
- 1.6 ZILOG Z80 1.17
- 1.7 MOTOROLA 6800 1.21
- 1.8 INTEL 8086 Microprocessor 1.25
 - 1.8.1 Pins and Signals of INTEL 8086 1.26
 - 1.8.2 Common Signals 1.28
 - 1.8.3 Minimum Mode Signals 1.29
 - 1.8.4 Maximum Mode Signals 1.30
 - 1.8.5 Architecture of INTEL 8086 1.31
 - 1.8.6 8086 Flag Register 1.34
 - 1.8.7 Instruction and Data Flow in 8086 1.34
- 1.9 MOTOROLA MC68000 1.35
 - 1.9.1 Pins and Signals of 68000 1.36
 - 1.9.2 Architecture of a MC68000 Microprocessor 1.39
 - 1.9.3 Programming Model of a 68000 Microprocessor 1.41
- 1.10 Short-Answer Questions 1.42
- 1.11 Exercises 1.50

CHAPTER 2: Introduction to Microcontrollers**2.1–2.56**

- 2.1 Introduction to Microcontrollers 2.1
 - 2.1.1 Comparison of Microprocessors and Microcontrollers 2.1
 - 2.1.2 Functional Building Blocks of a Microcontroller 2.2
- 2.2 INTEL 8051 Microcontroller 2.3
 - 2.2.1 Pins and Signals of 8051 2.3
 - 2.2.2 Architecture of 8051 2.7
 - 2.2.3 Programming Model of 8051 2.10
 - 2.2.4 Special Function Registers (SFR) of 8051 2.11
 - 2.2.5 IO Pins, Ports and Circuits 2.17
- 2.3 INTEL 8096 Microcontroller 2.20
 - 2.3.1 Pins and Signals of INTEL 8096 2.21
 - 2.3.2 Architecture of an 8096 Microcontroller 2.25
 - 2.3.3 Special Function Registers (SFR) of 8096 2.33
- 2.4 Introduction to PIC Microcontroller 2.41
 - 2.4.1 PIC16F877A Microcontroller 2.42
 - 2.4.2 Architecture of PIC16F877A 2.42
- 2.5 Introduction to ARM 2.44
 - 2.5.1 ARM7 Processor Core 2.45
 - 2.5.2 Comparison of PIC and ARM Controller 2.48
- 2.6 Short-Answer Questions 2.49
- 2.7 Exercises 2.52

CHAPTER 3: Instruction Set of 8085**3.1–3.68**

- 3.1 Timing Diagram of 8085 3.1
 - 3.1.1 Processor Cycles 3.1
 - 3.1.2 Machine Cycles of 8085 3.1
 - 3.1.3 Opcode Fetch Cycle of 8085 3.2
 - 3.1.4 Memory Read Cycle of 8085 3.2
 - 3.1.5 Memory Write Cycle of 8085 3.3
 - 3.1.6 IO Read Cycle of 8085 3.4
 - 3.1.7 IO Write Cycle of 8085 3.4
 - 3.1.8 Interrupt Acknowledge Cycle of 8085 3.5
 - 3.1.9 Interrupt Acknowledge Cycle of 8085 with RST n Instruction 3.5
 - 3.1.10 Interrupt Acknowledge Cycle of 8085 with CALL Instruction 3.7
 - 3.1.11 Bus Idle Cycle 3.9
 - 3.1.12 Machine Cycle with Wait States 3.9

3.2	Instruction Format of 8085	3.11	
3.3	Addressing Modes	3.11	
3.4	Classification of 8085 Instructions	3.12	
3.5	Data Transfer Instructions	3.21	
3.6	Data Manipulation and Control Instructions	3.29	
3.6.1	Arithmetic Instructions	3.29	
3.6.2	Logical Instructions	3.36	
3.6.3	Branching Instructions	3.43	
3.6.4	Machine Control Instructions	3.46	
3.7	Timing Diagram of 8085 Instructions		3.48
3.7.1	Timing Diagram of STA Instruction	3.49	
3.7.2	Timing Diagram of PUSH Instruction	3.50	
3.7.3	Timing Diagram of IN Instruction	3.51	
3.7.4	Timing Diagram of OUT Instruction	3.52	
3.7.5	Timing Diagram of INR M Instruction	3.53	
3.7.6	Timing Diagram of CALL Instruction	3.54	
3.7.7	Timing Diagram of RET Instruction	3.56	
3.8	Short-Answer Questions	3.57	
3.9	Exercises	3.64	

CHAPTER 4: Instruction Set of 8086**4.1–4.94**

4.1	Bus Cycles and Timing Diagram	4.1
4.1.1	Timing Diagram	4.2
4.1.2	Memory Read Cycle of 8086	4.2
4.1.3	Memory Write Cycle of 8086	4.2
4.1.4	IO Read Cycle of 8086	4.5
4.1.5	IO Write Cycle of 8086	4.6
4.1.6	Interrupt Acknowledge Cycle of 8086	4.7
4.2	Classification of 8086 Instructions	4.9
4.3	Format of 8086 Instructions	4.9
4.3.1	Addressing Modes of 8086	4.15
4.4	Instruction Execution Time	4.20
4.5	Instructions Affecting Flags of 8086	4.35
4.6	Explanation of 8086 Instructions	4.37
4.6.1	Data Transfer Instructions	4.38
4.6.2	Arithmetic Instructions	4.43
4.6.3	Logical Instructions	4.53

- 4.6.4 String-Manipulation Instructions 4.61
- 4.6.5 Control-Transfer Instructions 4.65
- 4.6.6 Processor-Control Instructions 4.74
- 4.7 Examples of 8086 Assembly Language Instructions 4.76
- 4.8 Short-Answer Questions 4.85
- 4.9 Exercises 4.90

CHAPTER 5: Instruction Set of 8051**5.1–5.40**

- 5.1 Machine Cycles and Timing Diagram 5.1
 - 5.1.1 External Program Memory Fetch Cycle 5.2
 - 5.1.2 External Data Memory Read Cycle 5.3
 - 5.1.3 External Data Memory Write Cycle 5.4
 - 5.1.4 Port Operation Cycle 5.5
- 5.2 Timing Diagram of 8051 Instructions 5.5
 - 5.2.1 Timing Diagram of MOVX A, @DPTR 5.7
 - 5.2.2 Timing Diagram of ADD A, #DATA 5.7
- 5.3 Addressing Modes 5.8
- 5.4 Instructions Affecting Flags of 8051 5.10
- 5.5 Classification of 8051 Instructions 5.11
- 5.6 Data Transfer Instructions 5.17
- 5.7 Data Manipulation Instructions 5.21
 - 5.7.1 Arithmetic Instructions 5.21
 - 5.7.2 Logical Instructions 5.23
- 5.8 Control Instructions 5.26
 - 5.8.1 Program Branching Instructions 5.27
 - 5.8.2 Boolean Instructions 5.30
- 5.9 IO Instructions 5.32
- 5.10 Comparison of 8085 and 8051 Assembly Language Programming 5.33
- 5.11 Short-Answer Questions 5.34
- 5.12 Exercises 5.36

CHAPTER 6: Memory and IO Interfacing**6.1–6.68**

- 6.1 Introduction to Memory 6.1
- 6.2 Semiconductor Memory 6.1
 - 6.2.1 ROM and PROM 6.3
 - 6.2.2 EPROM 6.4

- 6.2.3 Static RAM 6.8
- 6.2.4 DRAM 6.12
- 6.2.5 NVRAM 6.12
- 6.3 Interfacing Static RAM and EPROM 6.13
 - 6.3.1 Typical EPROM and Static RAM 6.13
 - 6.3.2 Memory Capacity 6.13
 - 6.3.3 Choice of Memory ICs and Address Allocation 6.14
 - 6.3.4 Generation of Chip Select Signals 6.15
 - 6.3.5 Decoder 6.16
- 6.4 Even and Odd Memory Banks in an 8086-Based System 6.17
- 6.5 Memory Organization in a Microcomputer System 6.19
 - 6.5.1 Memory Organization in an 8085-Based System 6.20
 - 6.5.2 Memory Organization in an 8086-Based System 6.24
 - 6.5.3 Memory Organization in an 8051-Based System 6.30
- 6.6 IO Structure of a Typical Microcomputer 6.32
 - 6.6.1 Interfacing IO and Peripheral Devices 6.33
 - 6.6.2 INTEL IO Port Devices 6.33
 - 6.6.3 INTEL Peripheral Devices 6.34
 - 6.6.4 IO Mapping 6.35
 - 6.6.5 IO Mapping in an 8085 Microprocessor-Based System 6.35
 - 6.6.6 IO Mapping in an 8086 Microprocessor-Based System 6.36
- 6.7 Memory and IO Interface Examples 6.38
 - 6.7.1 Examples of Memory and IO Interface in 8085-Based System 6.38
 - 6.7.2 Examples of Memory and IO Interface in 8086-Based System 6.51
 - 6.7.3 Examples of Memory and IO Interface in 8051-Based System 6.56
- 6.8 Short-Answer Questions 6.60
- 6.9 Exercises 6.65

CHAPTER 7: Interrupts**7.1–7.48**

- 7.1 Interrupt and its Need 7.1
 - 7.1.1 Interrupt Driven Data Transfer Scheme 7.1
- 7.2 Classification of Interrupts 7.2
- 7.3 Sources of Interrupts 7.3
 - 7.3.1 Sources of Interrupts in 8085 7.3
 - 7.3.2 Sources of Interrupts in 8086 7.3
 - 7.3.3 Sources of Interrupts in 8051 7.4
- 7.4 Interrupts of 8085 7.4
 - 7.4.1 Software Interrupts of 8085 7.4
 - 7.4.2 Hardware interrupts of 8085 7.5

- 7.4.3 Priorities of interrupts of 8085 7.6
- 7.4.4 Enabling, Disabling and Masking of 8085 Interrupts 7.6
- 7.4.5 INTR and its Expansion in 8085 7.8
- 7.5 Interrupts of 8086 7.10
 - 7.5.1 INTEL Predefined (or Dedicated) Interrupts 7.11
 - 7.5.2 Software Interrupts of 8086 7.12
 - 7.5.3 Hardware interrupts of 8086 7.12
 - 7.5.4 Priorities of interrupts of 8086 7.13
- 7.6 Implementing Interrupt Scheme in 8086 7.13
 - 7.6.1 Interrupt Vector Table 7.13
 - 7.6.2 Servicing an interrupt by 8086 7.15
 - 7.6.3 INTR and its Expansion in 8086 7.15
- 7.7 Programmable Interrupt Controller - INTEL 8259 7.17
 - 7.7.1 Interfacing 8259 with an 8085 Microprocessor 7.17
 - 7.7.2 Interfacing 8259 with an 8086 Microprocessor 7.19
 - 7.7.3 Functional Block Diagram of 8259 7.21
 - 7.7.4 Processing of Interrupts by 8259 7.23
 - 7.7.5 Programming (or initializing) 8259 7.25
 - 7.7.6 Initialization Command Words (ICWs) 7.25
 - 7.7.7 Operation Command Words (OCWs) 7.28
- 7.8 Interrupt Programming in 8051 7.29
 - 7.8.1 Interrupt Enable (IE) Register 7.29
 - 7.8.2 Interrupt Priority (IP) Register 7.30
 - 7.8.3 Handling Interrupts of 8051 7.30
 - 7.8.4 Examples of Interrupt Programming in 8051 Controller 7.31
- 7.9 Short-Answer Questions 7.36
- 7.10 Exercises 7.44

CHAPTER 8: Assembly Language Programming

8.1–8.214

- 8.1 Introduction to Assembly Language Programming 8.1
 - 8.1.1 Machine Level Programming 8.1
 - 8.1.2 Assembly Level Programming 8.1
 - 8.1.3 High Level Programming 8.2
- 8.2 Flowchart 8.2
- 8.3 Assembly Language Program Development Tools 8.3
 - 8.3.1 Editor (Text Editor) 8.4
 - 8.3.2 Assembler 8.4
 - 8.3.3 Library Builder 8.5
 - 8.3.4 Linker 8.5

- 8.3.5 Debugger 8.5
- 8.3.6 Simulator 8.6
- 8.3.7 Emulator 8.6
- 8.4 Variables and Constants used in Assemblers 8.8
- 8.5 Assembler Directives 8.9
- 8.6 Modular Programming 8.14
 - 8.6.1 Linking and Relocation 8.14
 - 8.6.2 Procedure (or) Subroutine 8.15
 - 8.6.3 Macros 8.17
 - 8.6.4 Delay Routine 8.17
 - 8.6.5 List and Array 8.21
- 8.7 Stack 8.21
 - 8.7.1 Stack in an 8085 Microprocessor 8.22
 - 8.7.2 Stack in an 8086 Microprocessor 8.22
 - 8.7.3 Stack in an 8051 Microcontroller 8.23
- 8.8 Byte and String Manipulation in 8086 8.24
 - 8.8.1 Byte Manipulation in 8086 8.24
 - 8.8.2 String Manipulation in 8086 8.24
- 8.9 Interrupts of Personal Computers 8.25
- 8.10 Assembly Language Format 8.31
- 8.11 Hand Coding of Assembly Language Programs in 8086 8.32
- 8.12 Examples of 8085 Assembly Language Programs 8.36
- 8.13 Examples of 8051 Assembly Language Programs 8.83
- 8.14 Examples of 8086 Assembly Language Programs 8.112
- 8.15 Short-Answer Questions 8.201
- 8.16 Exercises 8.206

CHAPTER 9: Peripheral Devices and Interfacing

9.1–9.180

- 9.1 Programmable Peripheral Devices 9.1
- 9.2 Parallel Data Communication Interface 9.1
 - 9.2.1 Parallel Data Transfer Schemes 9.2
 - 9.2.2 INTEL 8212 9.4
 - 9.2.3 Programmable IO Port and Timer - INTEL 8155/8156 9.6
 - 9.2.4 Programmable IO Port and Memory - INTEL 8355 9.12
 - 9.2.5 Programmable IO Port and Memory - INTEL 8755 9.13
- 9.3 Programmable Peripheral Interface - INTEL 8255 9.15
 - 9.3.1 Pins, Signals and Internal Block Diagram of 8255 9.16
 - 9.3.2 Interfacing of 8255 with 8085 Processor 9.17

-
- 9.3.3 Interfacing of 8255 with 8086 Processor 9.18
 - 9.3.4 Interfacing of 8255 with 8051 Microcontroller 9.19
 - 9.3.5 Programming (or initializing) 8255 9.21
 - 9.4 DMA Data Transfer Scheme 9.25
 - 9.4.1 A Microcomputer System with a DMA Controller 9.26
 - 9.5 DMA Controller - INTEL 8237 9.27
 - 9.5.1 Pins, Signals and Functional Block Diagram of 8237 9.29
 - 9.5.2 Internal Registers of 8237 9.32
 - 9.5.3 Programming (or initializing) 8237 9.36
 - 9.5.4 Interfacing of 8237 with 8085 Processor 9.37
 - 9.5.5 Interfacing of 8237 with 8086 Processor 9.39
 - 9.6 DMA Controller - INTEL 8257 9.43
 - 9.6.1 Pins, Signals and Functional Block Diagram of 8257 9.43
 - 9.6.2 Functional Block Diagram of 8257 9.45
 - 9.6.3 Interfacing of 8257 with 8085 Processor 9.48
 - 9.7 Serial Data Communication Interface 9.51
 - 9.7.1 Serial Data Communication 9.51
 - 9.7.2 RS-232C Serial Data Standard 9.53
 - 9.8 USART - INTEL 8251A 9.56
 - 9.8.1 Interfacing of 8251A with 8085 9.59
 - 9.8.2 Interfacing of 8251A with 8086 9.61
 - 9.9 Serial Communication in 8051 9.62
 - 9.9.1 Serial Data Buffer (SBUF) Register 9.63
 - 9.9.2 Power Control Register (PCON) 9.63
 - 9.9.3 Serial Port Control Register (SCON) 9.64
 - 9.9.4 Baud Rate in 8051 9.66
 - 9.9.5 Examples of Serial Port Programming in 8051 Controller 9.67
 - 9.10 Keyboard and Display Interface 9.70
 - 9.10.1 Keyboard Interface using 8255 Ports and 8085/8086 Processor 9.70
 - 9.10.2 Keyboard Interface using Ports of 8051 Controller 9.78
 - 9.10.3 Seven-Segment Display Interface using 8255 Ports and 8085/8086 Processor 9.82
 - 9.10.4 Latches and Buffers as IO Devices 9.89
 - 9.11 Keyboard/Display Controller - INTEL 8279 9.91
 - 9.11.1 Pins, Signals and Functional Block Diagram of 8279 9.91
 - 9.11.2 Keyboard and Display Interface using 8279 9.95
 - 9.11.3 Interfacing of 8279 with 8085 Processor 9.95
 - 9.11.4 Interfacing of 8279 with an 8086 Processor 9.98
 - 9.11.5 Interfacing of 8279 with in 8051 Microcontroller 9.98

- 9.12 Programmable Timer - INTEL 8254 9.101
 - 9.12.1 Pins, Signal and Functional Block Diagram of 8254 9.101
 - 9.12.2 Interfacing of 8254 with the 8085 Processor 9.103
 - 9.12.3 Interfacing of 8254 with the 8086 Processor 9.104
 - 9.12.4 Programming 8254 9.105
 - 9.12.5 Operating Modes of 8254 9.107
- 9.13 Programming 8051 Timers 9.113
 - 9.13.1 Timer Mode Control (TMOD) Register 9.114
 - 9.13.2 Timer Control (TCON) Register 9.115
 - 9.13.3 Calculating the Time Delay for 8051 Timers 9.116
 - 9.13.4 Examples of Timer Programming in an 8051 Controller 9.117
- 9.14 DAC Interface 9.120
 - 9.14.1 DAC0800 9.122
 - 9.14.2 Interfacing DAC0800 with 8085 9.124
 - 9.14.3 Interfacing DAC0800 with 8086 9.125
 - 9.14.4 Interfacing DAC0800 with 8051 9.126
 - 9.14.5 Programming the DAC interfaced (DAC0800) with 8051 9.128
- 9.15 ADC Interface 9.137
 - 9.15.1 ADC0809 9.138
 - 9.15.2 Interfacing ADC0809 with 8085 9.142
 - 9.15.3 Interfacing ADC0809 with 8086 9.143
 - 9.15.4 Interfacing ADC0809 with 8051 9.144
 - 9.15.5 Programming the ADC interfaced (ADC0809) with 8051 9.146
- 9.16 Liquid Crystal Display (LCD) 9.148
 - 9.16.1 Internal Architecture of LCD Controller-HD44780 9.152
 - 9.16.2 Pins and Signals of HD44780 LCD Display Module 9.155
 - 9.16.3 Interfacing HD44780 LCD Display Module to Microprocessor 9.157
 - 9.16.4 LCD Interfacing with the 8051 Microcontroller 9.165
- 9.17 Short-Answer Questions 9.169
- 9.18 Exercises 9.175

CHAPTER 10: Intel 80x86 Family of Processors**10.1–10.60**

- 10.1 Introduction 10.1
- 10.2 Intel 80186 Microprocessor 10.2
 - 10.2.1 Pins and Signals of 80186 10.3
 - 10.2.2 Architecture of 80186 10.7
- 10.3 Intel 80286 Microprocessor 10.10
 - 10.3.1 Pins and Signals of 80286 10.10
 - 10.3.2 Architecture of 80286 10.13

- 10.3.3 Real Address Mode of 80286 10.16
- 10.3.4 Protected Virtual Address Mode of 80286 10.16
- 10.4 Intel 80386 Microprocessor 10.20
 - 10.4.1 Pins and Signals of 80386 10.21
 - 10.4.2 Architecture of 80386 10.25
 - 10.4.3 Registers of 80386 Microprocessor 10.27
 - 10.4.4 Operating Modes of 80386 Microprocessor 10.30
- 10.5 Intel 80486 Microprocessor 10.34
 - 10.5.1 Pins and Signals of 80486 10.34
 - 10.5.2 Architecture of 80486 10.38
- 10.6 Pentium Microprocessor 10.40
 - 10.6.1 Pins and Signals of Pentium Microprocessor 10.40
 - 10.6.2 Architecture of Pentium Microprocessor 10.47
- 10.7 Advanced Pentium Microprocessors 10.49
 - 10.7.1 Pentium PRO 10.49
 - 10.7.2 Pentium II 10.50
 - 10.7.3 Pentium III 10.50
 - 10.7.4 Pentium 4 10.51
- 10.8 Short-Answer Questions 10.52
- 10.9 Exercises 10.55

CHAPTER 11: Microprocessor and Microcontroller-Based System Design 11.1–11.68

- 11.1 Designing a Microprocessor-Based System 11.1
- 11.2 Designing a Microcontroller-Based System 11.3
- 11.3 8085-Based Minimum System 11.5
- 11.4 Support Chips Needed for 8086 Microprocessor-Based System 11.7
 - 11.4.1 Clock Generator - INTEL 8284A 11.7
 - 11.4.2 Bus Controller - INTEL 8288 11.9
 - 11.4.3 Coprocessor - INTEL 8087 11.11
- 11.5 Basic Configurations of 8086 Microprocessor-Based System 11.14
 - 11.5.1 Minimum Mode 8086 Microprocessor System 11.14
 - 11.5.2 Maximum Mode 8086 Microprocessor System 11.15
- 11.6 Multiprocessor Configurations of 8086 Microprocessor-Based System 11.17
 - 11.6.1 Closely Coupled Configuration 11.18
 - 11.6.2 Loosely Coupled Configuration 11.18
- 11.7 Application to Automation Systems 11.20
 - 11.7.1 Sensor Interface for Automation System 11.20

11.8	Temperature Control System	11.23
11.8.1	Temperature Control System using 8085/8086 Processor	11.23
11.8.2	Interfacing Temperature Sensor with the 8051 Microcontroller	11.25
11.9	Motor Speed Control System using 8085/8086/8051	11.28
11.10	Traffic Light Control System	11.30
11.10.1	Traffic Light Control System using 8085/8086 Processor	11.30
11.10.2	Traffic Light Control System using 8051 Controller	11.36
11.11	Stepper Motor Control System	11.39
11.11.1	Stepper Motor Control System using 8085/8086 Processor	11.39
11.11.2	Stepper Motor Control System using the 8051 Microcontroller	11.43
11.12	Alarm Controller	11.47
11.12.1	Alarm Controller using 8085/8086 Processor	11.47
11.12.2	Alarm Controller using 8051 Controller	11.53
11.13	Servo Motor	11.55
11.13.1	Speed Control of Servo Motor	11.56
11.13.2	Servo Motors with Inbuilt Control Circuit	11.56
11.13.3	Angular Motion Control of Servo Motor	11.57
11.14	Short-Answer Questions	11.62
11.15	Exercises	11.65

Appendices**A.1–A.24**

APPENDIX I	List of Microprocessors Released by INTEL	A.1
APPENDIX II	8051 Instructions in Hexadecimal Order	A.3
APPENDIX III	8051 Instructions in Alphabetical Order	A.5
APPENDIX IV	8085 Instructions in Hexadecimal Order	A.7
APPENDIX V	8085 Instructions in Alphabetical Order	A.9
APPENDIX VI	Templates for 8086 Instructions	A.11
APPENDIX VII	DOS and BIOS Interrupts	A.21

General Index**I.1–I.10****Chip Index****I.1–I.3**