



Contents

<i>Preface</i>	<i>v</i>	
1. Introduction to Microwaves	1–14	
1.1 Introduction	1	
1.2 Propagation of Electromagnetic Waves	1	
1.3 Properties of Radio Waves	1	
1.4 Generation of Radio Waves	4	
1.5 Modulation	4	
1.6 Nature of Modulated Wave	4	
1.7 Significance of Sidebands	5	
1.8 Transmission of Radio Signals	6	
1.9 Reception of Radio Signals	6	
1.10 Detection of Radio Signals	6	
1.11 Reproduction of Radio Signals	7	
1.12 Microwave Frequencies	7	
1.13 Characteristics of Microwaves	8	
1.14 Microwave Devices	8	
1.15 Microwave Systems	9	
1.16 Microwave Units	9	
1.17 Historical Background	9	
1.18 Microwave Applications	10	
2. Transmission Line Theory and Impedance Matching	15–55	
2.1 Introduction	15	
2.2 Transmission Line Equations with Sinusoidal Excitation	15	
2.3 Transmission Line Constants	16	
2.4 Impedance and Admittance Equations	19	
2.5 Reflection Coefficient	22	
2.6 Transmission Coefficient	24	
2.7 Standing Wave	26	
2.8 Standing Wave Ratio (SWR)	29	
2.9 Smith Chart	32	
2.10 Impedance Matching	36	
2.11 Condition for Impedance Matching	36	
2.12 Impedance Matching Methods	36	
3. Multiconductor Microwave Transmission Lines	56–79	
3.1 Introduction	56	
3.2 Classification of MW Transmission Lines	56	
3.3 Coaxial Cables	57	
3.4 Lossless or Ideal Coaxial Lines	58	
3.5 Coaxial Cable Connectors and Adaptors	60	
3.6 Dielectric Bead Supports	62	
3.7 Planar Transmission Lines	64	
3.8 Strip Lines	64	
3.9 Microstrip Lines	66	
3.10 Parallel Strip Lines	70	
3.11 Slot Lines	72	
3.12 Shielded Strip Lines	72	
3.13 Coplanar Strip Lines	72	
4. Single Line and Open-Boundary Structures	80–116	
4.1 Introduction	80	
4.2 Waveguides	80	
4.3 Rectangular Waveguide	81	
4.4 Circular Waveguides	93	
4.5 Power Handling Capabilities	104	
4.6 Some Special Configurations of Waveguides	105	
4.7 Open-boundary Structures or Surface Waveguides	109	
4.8 Dielectric Rod Waveguides	109	
4.9 Dielectric Sheet on Conducting Plane	110	
4.10 Dielectric-Coated Conducting Cylinder or Goubau Line	110	
4.11 Comparison between Coaxial Lines and Waveguides	111	
4.12 Comparison of Various Transmission Lines	111	
5. Microwave Network Theory	117–134	
5.1 Introduction	117	
5.2 Electrical Network Parameters	117	
5.3 Symmetrical Property of Reciprocal Network	119	
5.4 Scattering Matrix of a Multi-Port Network	119	
5.5 Losses in Microwave Circuits	123	
5.6 Properties of S-matrix	123	
5.7 S-matrix of a Two-Port Network with Mismatched Load	126	
5.8 Comparison between S, Z and Y Parameters	127	
5.9 Advantages of S-matrix over Z and Y Matrices	128	

- 5.10 Derivation of Relationship between S , Z , Y and $ABCD$ Parameters 128

6. Microwave Passive Components 135–154

- 6.1 Introduction 135
- 6.2 Waveguide Choke Flanges 135
- 6.3 Short Circuit Plunger 136
- 6.4 Rectangular to Circular Waveguide Transition 137
- 6.5 Waveguide Corners, Bends and Twists 138
- 6.6 Coaxial Line to Waveguide Adaptors 138
- 6.7 Coupling Loops 139
- 6.8 Coupling Apertures 139
- 6.9 Attenuators 140
- 6.10 Phase Shifters 141
- 6.11 Waveguide Tees 143
- 6.12 Applications of Magic Tee 148

7. Microwave Isolators, Circulators and Directional Couplers 155–179

- 7.1 Introduction 155
- 7.2 Isolator or Uniline 155
- 7.3 Circulators 158
- 7.4 Three-Port Circulator 160
- 7.5 Directional Couplers 160
- 7.6 Types of Directional Couplers 162
- 7.7 Single-Hole or Bethe-Hole Coupler 162
- 7.8 Center-Hole Coupler 162
- 7.9 Offset-Hole Coupler 163
- 7.10 Two-Hole Coupler 163
- 7.11 Multi-Hole Coupler 164
- 7.12 S -matrix of a Directional Coupler 164
- 7.13 Binomial Coupler 165
- 7.14 Tchebyshev Coupler 167
- 7.15 Coupled Transmission Line Coupler 168
- 7.16 Multi-Section Coupler 168
- 7.17 Branch Line Coupler 169
- 7.18 Hybrid Ring or Rat-Race Coupler 169
- 7.19 Schwinger Reversed-Phase Coupler 170
- 7.20 Long Slot Coupler 171
- 7.21 Lange Directional Coupler 171
- 7.22 Capacitance Loop Coupler 171
- 7.23 Applications of Directional Couplers 171
- 7.24 Power Dividers and Combiners 172

8. Microwave Resonators 180–198

- 8.1 Introduction 180
- 8.2 Resonator Parameters 180
- 8.3 Resonator Types 181
- 8.4 Coaxial Cavity Resonator 181
- 8.5 Waveguide Cavity Resonators 183

- 8.6 Quality Factor of Cavities 188
- 8.7 Shunt Impedance of Cavity Resonators 192

9. Microwave Filters 199–222

- 9.1 Introduction 199
- 9.2 Classification of Filters 199
- 9.3 Filter Parameters 201
- 9.4 Insertion Loss Due to Mismatch 201
- 9.5 Microwave Filter Elements 202
- 9.6 Microwave Filter Design Techniques 202
- 9.7 Transformation of Prototype Filter 207
- 9.8 Design of MW Low-Pass Filter 209
- 9.9 Design of MW High-Pass Filter 210
- 9.10 Design of MW Band-Pass Filter 211
- 9.11 Microwave Band Stop Filter Design 213

10. Klystron Amplifier 223–246

- 10.1 Introduction 223
- 10.2 Limitations of Conventional Vacuum Tubes 223
- 10.3 Classification of Microwave Vacuum Tubes 225
- 10.4 Two Cavity Klystron Amplifier 225
- 10.5 Mechanism of Operation 226
- 10.6 Analysis of Two Cavity Klystron Amplifier 227
- 10.7 Beam Loading 233
- 10.8 Output Power 233
- 10.9 Typical Characteristics 234
- 10.10 Mutual Conductance 235
- 10.11 Voltage Gain 235
- 10.12 Applications of Two-Cavity Klystron Amplifier 235
- 10.13 Modern Klystron Tubes 235
- 10.14 Multi Cavity Klystron 237
- 10.15 Space-Charge Effects in Two Cavity Klystron 239

11. Reflex Klystron Oscillator 247–256

- 11.1 Introduction 247
- 11.2 Reflex Klystron Tube 247
- 11.3 Velocity Modulation 248
- 11.4 Oscillation Modes 249
- 11.5 Analysis of Reflex Klystron Oscillator 249
- 11.6 Equivalent Circuit 251
- 11.7 Electronic Admittance 251
- 11.8 Power Output 252
- 11.9 Efficiency 253
- 11.10 Mode Curves 253
- 11.11 Typical Characteristics 253
- 11.12 Reflex Klystron Modulators 253
- 11.13 Applications 254

12. Travelling Wave Tube Amplifier	257–271	15.10 Microwave Generation and Amplification 318
12.1 Introduction 257		16. Avalanche Transit Time Devices
12.2 Traveling Wave Tube (TWT) 257		325–340
12.3 Slow-Wave Structure Analysis 257		16.1 Introduction 325
12.4 Brillouin Diagram 258		16.2 Avalanche Transit Time Devices (ATTD) 325
12.5 Amplification Process 260		16.3 Read Diode 326
12.6 Suppression of Oscillations 267		16.4 IMPATT Diodes 329
12.7 Bandwidth 267		16.5 TRAPATT Diodes 333
12.8 Distortion 267		16.6 BARITT Diodes 335
12.9 Typical Characteristics 267		16.7 Comparison between TED and ATTD 336
12.10 Applications 268		17. Tunnel Diodes
12.11 Advantages 268		341–348
12.12 Comparison between TWT and Klystron Amplifiers 268		17.1 Introduction 341
13. Magnetron Oscillator	272–293	17.2 Tunnel Diode 341
13.1 Introduction 272		17.3 Tunnel Diode Amplifier 344
13.2 Types of Cross-Field Tubes 273		17.4 Tunnel Diode Oscillator 344
13.3 Magnetron Oscillators 273		17.5 Comparison between Tunnel Diodes and pn Junction Diode 345
13.4 Cylindrical Magnetron Oscillators 273		17.6 Applications 346
13.5 Linear Magnetron 279		18. Varactor Diodes
13.6 Coaxial Magnetron 282		349–354
13.7 Voltage-Tunable Magnetron 283		18.1 Introduction 349
13.8 Rieke Diagram 284		18.2 Principle of Operation 349
13.9 Amplitron (BWCFA) 284		18.3 Structure and Equivalent Circuit 350
13.10 Carcinotron (BWCFO) 287		18.4 Varactor Diode Frequency Multiplier 351
14. Microwave Crystal, Schottky and PIN Diodes	294–303	18.5 Varactor Diode Tuning Circuit 352
14.1 Introduction 294		18.6 Applications 352
14.2 Classification of Microwave Diodes 294		19. Parametric Amplifiers
14.3 Crystal Diode 294		355–364
14.4 Schottky Diode 295		19.1 Introduction 355
14.5 Applications 296		19.2 Principle of Parametric Amplifier 355
14.6 PIN Diode 297		19.3 Manley-Rowe Power Relations 355
14.7 PIN Diode Applications 298		19.4 Power Output 357
15. Transferred Electron (Gunn) Devices	304–324	19.5 Power Gain 357
15.1 Introduction 304		19.6 Parametric Amplifiers 357
15.2 Bulk Negative Resistance 304		19.7 Up-Converter 358
15.3 Gunn Effect and GaAs Diode 305		19.8 Down-Converter 358
15.4 Ridley-Watkins-Hilsum (RWH) Theory 306		19.9 Negative Resistance Parametric Amplifier 359
15.5 Equivalent Circuit 313		19.10 Degenerate Parametric Amplifier 360
15.6 Modes of Operation 313		19.11 Advantages of Up-Converters 360
15.7 LSA Diodes 315		19.12 Advantages and Limitations of Parametric Amplifiers 361
15.8 INP Diodes 317		19.13 Applications 361
15.9 CdTe Diodes 318		20. Microwave Transistors
		365–377
		20.1 Introduction 365
		20.2 High-Frequency Limitations 365
		20.3 Bipolar Junction Transistors 366
		20.4 CE Configuration 367

20.5 CB Configuration 367	
20.6 Transistor Biasing 368	
20.7 Internal Tuning of Microwave Transistors 368	
20.8 Typical Characteristics 369	
20.9 Comparison between SI and GaAs Microwave Transistors 369	
20.10 Microwave Field Effect Transistors 369	
20.11 Cut-Off Frequency and Maximum Oscillation Frequency 370	
20.12 High Electron Mobility Transistor 371	
20.13 FET Biasing 371	
20.14 Microwave Transistor Amplifier Circuit 372	
20.15 Microwave Transistor Oscillator Circuit 372	
20.16 Applications of Microwave Transistors 372	
20.17 Transistor Noise Factor 373	
20.18 Equivalent Noise Temperature 374	
21. Microwave Communication Systems	378–390
21.1 Introduction 378	
21.2 Basic Microwave Communication Systems 378	
21.3 Terminal Stations 379	
21.4 Microwave Frequency Scheme 380	
21.5 Microwave Repeaters 380	
21.6 Atmospheric Refraction 381	
21.7 Radio Horizon 382	
21.8 Contour Maps 383	
21.9 Fresnel Zone 383	
21.10 Ground Reflections 384	
21.11 Super-refraction and Subrefraction 384	
21.12 Fading 385	
21.13 Diversity Systems 386	
21.14 Microwave Link Design 386	
21.15 System Gain 386	
21.16 Advantages of Microwave Communication Systems 387	
22. Satellite Communication Systems	391–398
22.1 Introduction 391	
22.2 Communication Satellites 391	
22.3 Satellite Communication Systems 392	
22.4 Ground Station 392	
22.5 Satellite Transponder 393	
22.6 Link Losses 394	
22.7 Link Budget Calculations 395	
23. Radar Systems	399–412
23.1 Introduction 399	
23.2 Radar Classification 399	
23.3 Radar Frequencies 400	
23.4 Basic Radar System 400	
23.5 Radar Range Equations 400	
23.6 Duplexer 402	
23.7 Pulsed Radar 403	
23.8 FMCW Radar 405	
23.9 Doppler Effect 406	
23.10 FM Doppler Radar 406	
23.11 CW Doppler Radar 407	
24. Industrial Applications of Microwaves	413–420
24.1 Introduction 413	
24.2 Microwave Heating 413	
24.3 Domestic Microwave Ovens 414	
24.4 Industrial Microwave Dryers 415	
24.5 Industrial Plasma Generators 416	
24.6 Measurement of Moisture Content 416	
24.7 Measurement of Thickness 417	
24.8 Microwave Applications in Medicine 417	
25. Monolithic Microwave Integrated Circuits	421–438
25.1 Introduction 421	
25.2 Classification 421	
25.3 Scale of Integration 422	
25.4 Applications 422	
25.5 Materials for MMIC Fabrication 422	
25.6 Properties of Substrate Materials 423	
25.7 Selection of Substrate Materials 423	
25.8 Properties of Conductive Materials 423	
25.9 Properties of Dielectric Materials 424	
25.10 Properties of Resistive Materials 425	
25.11 Development of Microwave Integrated Circuits (MMICs) 425	
25.12 Monolithic Microwave Integrated Circuits 425	
25.13 MMIC Fabrication Methods 426	
25.14 Example of Fabrication 428	
25.15 Disadvantages of MMICs 428	
25.16 Fabrication of MOSFET 428	
25.17 Thick-Film Formation 431	
25.18 Hybrid Microwave Integrated Circuit (HMIC) Fabrication 434	
25.19 Quasimonolithic Microwave Integrated Circuits (QMMICs) 436	

26. Microwave Measurement Devices and Instruments 439–446

- 26.1 Introduction 439
- 26.2 Tunable Detector 439
- 26.3 Slotted Line Probe 440
- 26.4 VSWR Meter 441
- 26.5 Spectrum Analyzer 442
- 26.6 Network Analyzer 443
- 26.7 MW Reference Power Sensors 444
- 26.8 MW Power Sensors 444

27. Microwave Measurement Techniques 447–463

- 27.1 Introduction 447
- 27.2 Microwave Power Measurements 447
- 27.3 Insertion Loss and Attenuation Measurements 449
- 27.4 VSWR Measurements 449
- 27.5 Impedance Measurements 451
- 27.6 Measurement of Scattering Parameters 452
- 27.7 Measurement of Frequency 452
- 27.8 Measurement of Cavity Q 454
- 27.9 Measurement of Dielectric Constant 456
- 27.10 Measurement of Antenna Parameters 458
- 27.11 Measurement of Noise Factor 460

28. Microwave Radiation Hazards 464–471

- 28.1 Introduction 464
- 28.2 Features of Microwave Radiation 464
- 28.3 Microwave Radiation Levels 464
- 28.4 Biological Interactions 465
- 28.5 Interactive Mechanisms 467
- 28.6 Biological Effects 467
- 28.7 Hazard Levels and Protection 468

29. Microwave Antennas 472–489

- 29.1 Introduction 472
- 29.2 Antenna Characteristics 472

- 29.3 Antenna Efficiency 472
- 29.4 Antenna Gain 473
- 29.5 Radiation Pattern and Side Lobes 474
- 29.6 Beam Width 475
- 29.7 Polarization 475
- 29.8 Classification of Antennas 477
- 29.9 Half-Wave Dipole Antenna 477
- 29.10 Horn Antennas 479
- 29.11 Reflector Antenna 481
- 29.12 Lens Antennas 483
- 29.13 Slot Antennas 484
- 29.14 Microstrip Antennas 484
- 29.15 Semiconductor Dipole Antennas 486

Glossary 490–498

Appendices 499–506

Appendix I: University Question Papers 499

Appendix II: Classification of Microwave Solid State Devices 503

Appendix III: Applications of MW Solid State Devices 503

Appendix IV: Standard Multiples and Sub-multiples 504

Appendix V: Greek Letters 504

Appendix VI: Physical Constants 504

Appendix VII: Properties of Free Space 504

Appendix VIII: Pascal's Triangle 505

Appendix IX: Characteristics of Single Stage Solid State MW Amplifiers 505

Appendix X: Electromagnetic Frequency Spectrum 505

Appendix XI: Visible Spectrum 506

Appendix XII: Television Channels 506

Index 507–511