

Contents

<i>Preface to the Fifth Edition</i>	v
<i>Preface to the First Edition</i>	vii
1 Load Characteristics	1 – 15
1.1 Introduction 1	
1.2 Advantages of electrical energy 1	
1.3 Load 1	
1.4 Connected load 2	
1.5 Demand 2	
1.6 Demand interval 2	
1.7 Maximum demand (MD) or peak load 2	
1.8 Demand factor (DF) 2	
1.9 Average load or average demand 3	
1.10 Load factor 3	
1.11 Diversity factor F_D 3	
1.12 Load diversity 4	
1.13 Utilization factor F_u 4	
1.14 Plant factor or capacity factor 4	
1.15 Loss factor F_{LS} 5	
1.16 Load curve 5	
1.17 Informations obtained from load curves 5	
1.18 Utility of load curves 6	
1.19 Load-duration curve 6	
1.20 Procedure for plotting the load-duration curve 6	
1.21 Informations available from load duration curve 6	

2	Supply Systems	16 – 35
2.1	Introduction	16
2.2	Basic structure of an AC power system	16
2.3	Distribution voltage level	16
2.4	Subtransmission level	17
2.5	Transmission level	17
2.6	Layout of a power supply network	17
2.7	System interconnection	18
2.8	System voltage and transmission efficiency	19
2.9	Working voltage	20
2.10	Choice of the next high voltage	20
2.11	Standardization of transmission voltages	21
2.12	Classification of lines	21
2.13	Comparison of conductor costs in various systems	22
2.13.1	Criterion of equal maximum voltage to earth	23
2.13.2	Criterion of equal maximum voltage between line conductors	27
3	Conductors	36 – 54
3.1	Introduction	36
3.2	Types of conductors	37
3.2.1	Hard-drawn copper conductors	37
3.2.2	Cadmium copper conductor	37
3.2.3	Steel-cored copper conductor (SCC)	38
3.2.4	Copperweld conductor	38
3.2.5	Hard-drawn aluminium conductor or all-aluminium conductor (AAC)	38
3.2.6	Aluminium conductor steel reinforced (ACSR)	38
3.2.7	Smooth body ACSR conductor	39
3.2.8	Expanded ACSR conductor	40
3.2.9	All-aluminium alloy conductor (AAAC)	40
3.2.10	ACAR conductor	40
3.2.11	Alumoweld conductor	41
3.2.12	Phosphor-bronze conductor	41
3.2.13	Galvanized steel conductor	41
3.3	Resistance	41
3.4	Skin effect	42
3.5	Equivalent copper section	43
3.6	Kelvin's economy law	43
3.7	Modified Kelvin's law	44
3.8	Graphical representation	45
3.9	Economic current density	46
3.10	Determination of losses	49
3.11	Limitations of Kelvin's law	52

4	Power Cables	55 – 92
4.1	Introduction	55
4.2	Cable construction	56
4.3	Conductors	56
4.4	Insulation	57
4.5	Sheath	58
4.6	Protective covering	58
4.7	Belted cable	59
4.8	Screened cable	59
4.9	Cable impregnation	60
4.10	Non-drained cables	60
4.11	Dielectric stress	60
4.12	Grading of cables	64
4.13	Cable capacitance	70
4.14	Charging current or capacitive current	70
4.15	Capacitances in a three-core belted cable	70
4.16	Measurement of C_c and C_s	72
4.17	Insulation resistance	74
4.18	Dielectric loss	75
	4.18.1 Conductivity of insulation	75
	4.18.2 Dielectric hysteresis or dielectric absorption	75
	4.18.3 Corona or gaseous ionization in cables	76
	4.18.4 Dielectric power loss	76
4.19	Stress distribution in a HVDC cable	78
4.20	Skin effect	79
4.21	Proximity effect	79
4.22	Current rating of cables	79
	4.22.1 Normal or safe current carrying capacity	79
	4.22.2 Over current rating	81
	4.22.3 Short-circuit rating	82
4.23	Thermal breakdown	82
4.24	Soil thermal resistivity	82
4.25	Extra high voltage cables	82
4.26	Oil-filled cables	83
	4.26.1 Advantages of self-contained oil-filled cables	85
	4.26.2 Advantages of oil-filled cables	85
	4.26.3 Oil for cables	85
4.27	Gas-pressure cables	86
	4.27.1 External gas-pressure cables	86
	4.27.2 Internal gas-pressure cables	86
4.28	Compressed gas insulated cables (GIC)	87
4.29	Advantages of GIC over oil-filled cables	88
4.30	Cross-linked polyethylene (XLPE) cables	89
4.31	Power cable installation	89

5	Line Insulators and Supports	93 – 122
5.	Introduction	93
5.2	Types of insulator	95
5.2.1	Pin type insulator	95
5.2.2	Suspension insulators	96
5.2.3	Strain or tension insulators	97
5.3	V-strings	98
5.4	Insulator materials	98
5.4.1	Polymer insulator	99
5.5	Voltage distribution and string efficiency	99
5.5.1	Alternative method	101
5.6	Improving voltage distribution	103
5.7	Selection of insulation	112
5.8	Line supports	113
5.9	Wood poles	114
5.10	Concrete poles	114
5.11	Steel poles	115
5.12	Supporting towers	115
5.12.1	Self-supporting towers	115
5.12.2	Guyed or stayed towers	115
5.13	Vibration of conductors	117
5.13.1	Resonant vibration	117
5.13.2	Galloping	118
5.13.3	Dancing and steel-jump	118
5.14	Effects of vibration on the transmission line	118
5.15	Prevention of vibration	119
5.15.1	Armour rods	119
5.15.2	Stockbridge damper	119
5.15	Spacing of conductors	120
6	Sag and Tension	123 – 150
6.1	Introduction	123
6.2	Sag and tension	123
6.3	Parabolic method	124
6.4	Catenary method	125
6.5	Accuracy of results	128
6.6	Loading on conductors	128
6.7	Conductor clearance from ground	131
6.8	Erection sag and tension	132
6.8.1	Factors affecting the sag	133
6.9	Spans of unequal length	137
6.10	Sag and tension charts	138
6.11	Supports at unequal levels	139
6.12	The sag template	144
6.13	Preparation of the sag template	145
6.14	Method of using the template	146
6.15	Economic span length	147

7	Line Parameters	151 – 212
7.1	Introduction	151
7.2	Line inductance	151
7.3	Inductance of a conductor	152
	7.3.1 Internal inductance	152
	7.3.2 External inductance	154
7.4	Flux linkages in a group of conductors	155
7.5	Inductance of a two-wire line	157
7.6	Inductance of symmetrical three-phase line	159
7.7	Inductance of unsymmetrical three-phase line	160
7.8	Method of geometric mean distances	163
7.9	Two-wire line	165
7.10	Symmetrical three-phase line	165
7.11	Inductance of unsymmetrical three-phase line	166
7.12	Inductance of double-circuit single-phase line	169
7.13	Inductance of double-circuit three-phase lines	170
7.14	Special cases of double-circuit lines	172
7.15	Inductance of bundled conductor lines	174
7.16	Line capacitance	178
7.17	Electric field of a long straight conductor	178
7.18	System of conductors	179
7.19	Capacitance of two-wire line	180
7.20	Capacitance of the symmetrical three-phase line	182
7.21	Capacitance of an unsymmetrical three-phase transposed line	183
7.22	Capacitance of a three-phase single-circuit untransposed line	186
7.23	Charging current	187
7.24	Capacitance by GMD method	188
7.25	Capacitance of double-circuit three-phase line	189
7.26	Effect of earth on the line capacitance	190
7.27	Effect of earth on capacitance of single-circuit three-phase line with transposition	193
7.28	Capacitance of bundled conductor lines	195
7.29	Shunt conductance	198
7.30	Interference between power and communication lines	198
7.31	Electromagnetic effect	198
7.32	Electrostatic effect	199
8	Per Unit Representation	213 – 237
8.1	Introduction	213
8.2	Change of base	216
8.3	Per unit impedance of a transformer	216
8.4	Per unit quantities in three-phase systems	219
8.5	Selection of base values	221
8.6	Base quantities in terms of kV and MVA	221
8.7	Per unit load impedance	222

8.8	Advantages of per unit representation	224
8.9	One-line diagrams	225
8.10	Preparation of impedance diagrams	226
9	Short and Medium Lines	238 – 265
9.1	Introduction	238
9.2	Classification of lines	238
9.3	Short single-phase line	239
9.4	Phasor diagram	240
9.5	Short three-phase line	241
9.6	Transmission line as a two-port network	242
9.6.1	ABCD constants of a short line	243
9.7	Line regulation	243
9.7.1	Line regulation for short lines	243
9.8	Line efficiency or transmission efficiency	244
9.9	Line with transformers	248
9.10	Medium lines	251
9.11	Nominal T model of a medium line	252
9.11.1	Phasor diagram	253
9.12	Nominal Π model of a medium line	254
9.12.1	Phasor diagram	255
9.13	Calculation of transmission efficiency and regulation of medium lines	256
10	Long Transmission Lines	266 – 282
10.1	Introduction	266
10.2	Exact solution of a long line	266
10.3	Physical interpretation of the long line equations	269
10.4	Propagation constant	270
10.5	Wavelength and velocity of propagation	271
10.6	Characteristic impedance Z_0	271
10.7	Hyperbolic form of line equations	272
10.8	Evaluation of ABCD parameters	273
10.9	Ferranti effect	278
10.10	Surge impedance loading (SIL)	279
11	General Network Constants	283 – 310
11.1	Introduction	283
11.2	Cascaded networks	284
11.3	Relations between ABCD constants	286
11.4	Output in terms of input	287
11.5	Typical transmission networks	288
11.5.1	Series impedance circuit	289
11.5.2	Shunt admittance circuit	289
11.5.3	Half T-network	289

11.5.4	T-network	290
11.5.5	Π -network	291
11.5.6	Ideal transformer	292
11.5.7	Actual transformer	292
11.5.8	Transmission line	293
11.5.9	Transmission line with transformers at both ends	294
11.6	Networks in parallel	296
11.7	Equivalent networks	298
11.8	Equivalent T-network of a line	298
11.9	Equivalent Π networks of a line	299
11.10	The nominal T- and Π -equivalent network of a line	299
11.11	Experimental determination of ABCD constants	300
12	Power Circle Diagrams	311
12.1	Introduction	311
12.2	Receiving-end voltage phasor diagram	311
12.3	Phasor volt-amperes	312
12.4	Receiving-end power circle diagram	312
12.5	Analytical method	316
12.6	Sending-end voltage phasor diagram	318
12.7	Sending-end power circle diagram	318
12.8	Analytical method	321
12.9	Power transmitted over a line	323
12.10	Per unit value circle diagrams	324
12.11	Receiving-end per unit circle diagrams	324
12.12	Sending-end per unit circle diagrams	326
12.13	Universal power circle diagrams	327
12.14	The use of universal power circle diagrams	328
13	Control of Voltage and Reactive Power	331
13.1	Introduction	331
13.2	Methods of voltage control	332
13.3	Tap-changing transformers	333
13.3.1	Off-load tap-changing transformer	333
13.3.2	On-load tap-changing transformer	333
13.4	Shunt reactors	335
13.5	Shunt capacitors	335
13.6	Series compensation	336
13.7	Location of series capacitors	337
13.8	Protective schemes for series capacitors	337
13.9	Problems associated with series capacitors	338
13.10	Series capacitor versus shunt capacitor	339
13.11	Synchronous phase modifiers	339
13.11.1	Rating of a phase modifier	340
13.12	Static VAR systems (SVS)	347

13.13	SVS schemes	348
13.14	Thyristor controlled reactor (TCR)	348
13.15	Thyristor switched capacitor (TSC)	348
13.16	FC-TCR type VAr compensator	349
13.17	TSC-TCR scheme	350
13.18	Advantages of SVS	351
13.19	Applications of SVS	351
14	Load Flow Analysis	354 – 383
14.1	Introduction	354
14.2	Load flow problem	354
14.3	Bus admittance matrix Y_{bus}	356
14.4	Static load flow equations (SLFE)	363
14.5	Methods of load flow solution	364
14.6	Gauss-Seidel method using Y_{bus}	364
14.6.1	Computation for load buses	366
14.6.2	Computation for PV buses	367
14.6.3	Acceleration factors	368
14.7	Newton-Raphson (NR) method	368
14.8	Newton-Raphson method for load flow solution	371
14.9	Computational procedure for Newton-Raphson method	374
14.10	Power flow through lines and slack bus power	376
14.11	Decoupled load flow methods	376
14.12	Fast decoupled load flow (FDLF) method	377
14.13	DC load flow method	378
14.14	Comparison of load flow analysis methods	379
15	Economic Operation of Power Systems	384 – 403
15.1	Introduction	384
15.2	Incremental fuel cost	385
15.3	Economic dispatch neglecting transmission losses	386
15.4	Transmission loss as a function of plant generation	391
15.5	General loss formula	393
15.6	Optimum load dispatch considering transmission losses	394
15.7	Iterative method of solving coordination equation	398
16	Symmetrical Faults	404 – 430
16.1	Introduction	404
16.2	Effects of faults	405
16.3	Purpose of fault analysis	405
16.4	Simplifying assumptions	405
16.5	Thevenin's equivalent circuit	406
16.6	Short-circuit capacity, SCC	406
16.7	Procedure for calculating short-circuit voltamperes and short-circuit current	408

16.8	Star-delta and delta-star transformations	408
16.9	Transient in a series R - L circuit	409
16.10	Sudden short-circuit at the armature terminals of a three-phase generator	411
16.11	Consideration of prefault load current	416
16.12	Current-limiting reactors	417
	16.12.1 Construction of reactors	417
	16.12.2 Location of reactors	417
	16.12.3 Rating of reactors	419
16.13	Short-circuit MVA in a tie-bus system	419
17	Symmetrical Components	431
17.1	Introduction	431
17.2	Fortescue's theorem	431
17.3	Phase sequence	431
17.4	α -operator	432
17.5	Symmetrical components of an unbalanced three-phase system	432
17.6	Component synthesis	433
17.7	Component analysis	434
17.8	Graphical method of determining sequence components	436
17.9	Symmetrical components of current phasors	436
17.10	Zero-sequence components of voltage	437
17.11	General nature of zero-sequence currents	438
17.12	Power in terms of symmetrical components	443
17.13	Potential of neutral	447
17.14	Phase shift in star-delta transformers	448
17.15	Sequence impedances	449
17.16	Sequence networks for fault calculations	450
17.17	Sequence impedances of a transmission line	451
17.18	Sequence impedances of synchronous machines	454
17.19	Sequence networks of synchronous machines	455
17.20	Zero-sequence networks of transformers	457
17.21	Assembly of sequence networks of a power system	459
18	Unsymmetrical Faults	463
18.1	Introduction	463
18.2	Assumptions	464
18.3	Sequence voltages of a generator	464
18.4	Sequence voltages at a fault point	464
18.5	General procedure	465
18.6	Single line-to-ground (LG) fault	466
18.7	Line-to-line fault	469
18.8	Double line-to-ground (LLG or DLG) fault	471
18.9	Balanced three-phase fault	474
18.10	Comparison of single line-to-ground and three-phase fault currents	480

18.11	Open conductor faults	482
18.11.1	One conductor open	482
18.11.2	Two conductors open	482
19	Power System Stability	486 – 536
19.1	Introduction	486
19.2	Stability limits and power transmission capability	487
19.3	Infinite bus	487
19.4	Synchronous generator connected to an infinite bus	488
19.5	Power-angle curve	489
19.6	Representation of a T-circuit with a series circuit	490
19.7	Power-angle relations for general network configurations	491
19.8	Transfer impedance	492
19.9	Power-angle characteristic of a salient-pole synchronous machine	498
19.10	Steady-state stability criterion	501
19.11	Transient stability	502
19.12	Swing equation	502
19.13	Swing curves	504
19.14	<i>M</i> and <i>H</i> constants	504
19.14.1	<i>M</i> constant	504
19.14.2	<i>H</i> constant or per unit inertia constant	505
19.14.3	<i>H</i> constant on a common base	506
19.15	Equivalent system	506
19.16	Equivalent <i>M</i> constant of two machines	506
19.17	Equal-area criterion of stability	509
19.17.1	Application to sudden increase in mechanical power input	511
19.17.2	One of the parallel lines suddenly switched off	515
19.18	System fault and subsequent circuit isolation	518
19.18.1	System fault, circuit isolation and reclosing	521
19.19	Numerical solution of swing equation (point-by-point solution)	525
19.20	Methods of improving stability	530
20	Travelling Waves	537 – 573
20.1	Introduction	537
20.2	Wave equation	537
20.3	Characteristic impedance	541
20.4	Energy and power of a surge	543
20.5	Evaluation of surge impedance	544
20.6	Velocity of travelling waves	545
20.7	Incident and reflected waves	546
20.8	Reflection of waves	547
20.9	Transmission or refraction of waves	548
20.10	Open-circuited line	549
20.11	Short-circuited line	551
20.12	Line terminated in Z_0	551

20.13	Series reactive termination	551
20.14	Parallel reactive termination	554
20.15	Line terminated in a capacitor	555
20.16	Junction of two dissimilar lines	556
20.17	Effect of cable on surge	560
20.18	Junction of several lines	561
20.19	Repeated reflections	563
21	Overvoltage Protection	574 – 588
21.1	Introduction	574
21.2	Internal overvoltages	574
21.3	External overvoltages	575
21.4	Mechanism of the lightning discharge	575
21.5	Frequency of lightning flashovers	576
21.6	Stroke currents	576
21.7	Direct and induced strokes	577
21.8	Wave shapes of stroke currents	577
21.9	Overvoltage protection	577
21.10	Overhead earth wire	578
21.11	Rod gap	579
21.12	Surge diverters	580
21.13	Expulsion-type surge diverter	580
21.14	Valve-type surge diverter	581
21.15	Metal-oxide gapless surge diverters	582
21.16	Advantages of ZnO diverters	584
21.17	Location of surge diverters	584
21.18	Selection of surge diverters	584
21.19	Lightning performance of lines	585
21.20	Basic impulse insulation level or basic insulation level (BIL)	585
21.21	Volt-time characteristic (curve)	585
21.22	Insulation coordination	586
22	Corona	589 – 607
22.1	Introduction	589
22.2	The phenomenon of corona	589
22.3	Theory of corona formation	590
22.4	The calculation of potential gradient	590
22.5	Factors affecting corona	595
22.6	Disruptive critical voltage	597
22.7	Visual critical voltage	599
22.8	Corona power loss	601
22.9	Radio and television interference (RI)	604
22.10	Minimizing corona	604
	22.10.1 Bundled conductors	605

23	High Voltage Direct Current (HVDC) Transmission	608 – 626
23.1	Introduction	608
23.2	Classification of HVDC systems	609
23.3	AC interconnection	612
23.3.1	Limitations of AC interconnection	612
23.3.2	Advantages of DC interconnection	613
23.4	Stability limits	613
23.5	HVDC cable transmission	613
23.6	Economic comparison	614
23.7	Conversion of three-phase AC line to DC line	615
23.8	Advantages of HVDC transmission	616
23.9	Economic distances for HVDC transmission	617
23.10	Components of an HVDC transmission system	618
23.11	Converter station	618
23.12	Converter unit	618
23.13	Converter valves	620
23.14	Converter transformers	620
23.15	Filters	621
23.15.1	AC filters	621
23.15.2	DC filters	621
23.15.3	High-frequency filters	621
23.16	Reactive power source	621
23.17	Smoothing reactor	621
23.18	HVDC system pole	622
23.19	Ground electrodes	622
23.20	Back-to-back HVDC station (HVDC coupling station)	622
23.21	Two-terminal HVDC system	623
23.22	Multiterminal DC (MTDC) system	623
23.22.1	Advantages of MTDC systems	623
23.22.2	Application of MTDC systems	623
23.23	DC circuit breakers	624
23.24	Limitations of HVDC transmission	624
23.25	Developments in DC technology	625
23.26	Applications of HVDC transmission	625
23.27	HVDC systems in India	625
24	System Neutral Grounding	627 – 638
24.1	Introduction	627
24.2	Ungrounded neutral system	627
24.3	Arcing grounds	629
24.4	Advantages of neutral grounding	629
24.5	Methods of neutral grounding	630
24.6	Solid grounding	630
24.7	Resistance grounding	631
24.8	Reactance grounding	632

24.9	Peterson coil grounding	632
24.9.1	Construction of Peterson coil	634
24.9.2	Rating of Peterson coil	634
24.9.3	Advantages of Peterson coil grounding	634
24.9.4	Limitations of Peterson coil grounding	634
24.10	Grounding transformer	634
24.11	Choice of grounding	636
25	Tariffs	639
25.1	Introduction	639
25.2	Types of tariffs	640
25.2.1	Flat demand rate tariff	640
25.2.2	Straight-line meter rate tariff	640
25.2.3	Block meter rate tariff	641
25.2.4	Two-part tariff	641
25.2.5	Power factor tariff	641
25.2.6	Seasonal rate tariff	642
25.2.7	Peak-load tariff	642
25.2.8	Three-part tariff	642
26	Power Factor Improvement	648
26.1	Introduction	648
26.2	Disadvantages of a low power factor	648
26.3	Causes of low power factor	649
26.4	Power factor improvement	650
26.5	Power factor correction by static capacitors	650
26.6	Capacitor rating calculations	651
26.7	Power factor correction in three-phase systems	654
26.8	Advantages and limitations of static capacitors	657
26.9	Location of capacitors	658
26.10	Power factor correction by synchronous motors	658
26.11	Economics of power factor improvement	661
26.11.1	Most economical power factor when kW demand is constant	662
26.11.2	Most economical power factor when kVA demand is constant	663
26.12	Economics of supply of increased power demand	664
27	Voltage Stability	671
27.1	Introduction	671
27.2	Classification of voltage stability	671
27.2.1	Large-distance voltage stability	672
27.2.2	Small-distance voltage stability	672
27.3	Rotor-angle stability and voltage stability	672
27.4	Voltage stability limit	672

27.5	Voltage stability analysis	674
27.5.1	P-V curves	674
27.5.2	V-Q curves	675
27.6	Methods of improving voltage stability	675
27.6.1	Reactive power compensation	675
27.6.2	Load shedding during contingencies	676
27.6.3	Use of LTC (load tap changing transformers)	677
28	Flexible AC Transmission Systems (FACTS)	678 – 683
28.1	Introduction	678
28.2	Basic types of FACTS controllers	679
28.2.1	Series controllers	680
28.2.2	Shunt controllers	680
28.2.3	Combined series-series controllers	680
28.2.4	Combined series-shunt controllers	680
28.3	STATCOM	680
28.4	Static synchronous generator (SSG)	680
28.5	Static synchronous series compensator (SSSC)	681
28.6	Interline power flow controller (IPFC)	681
28.7	Unified power flow controller (UPFC)	682
28.8	Thyristor-controlled phase shifting transformer (TCPST)	682
28.9	Interphase power controller (IPC)	682
28.10	Thyristor-controlled voltage limiter (TCVL)	683
Appendix		685
Index		687 – 694